
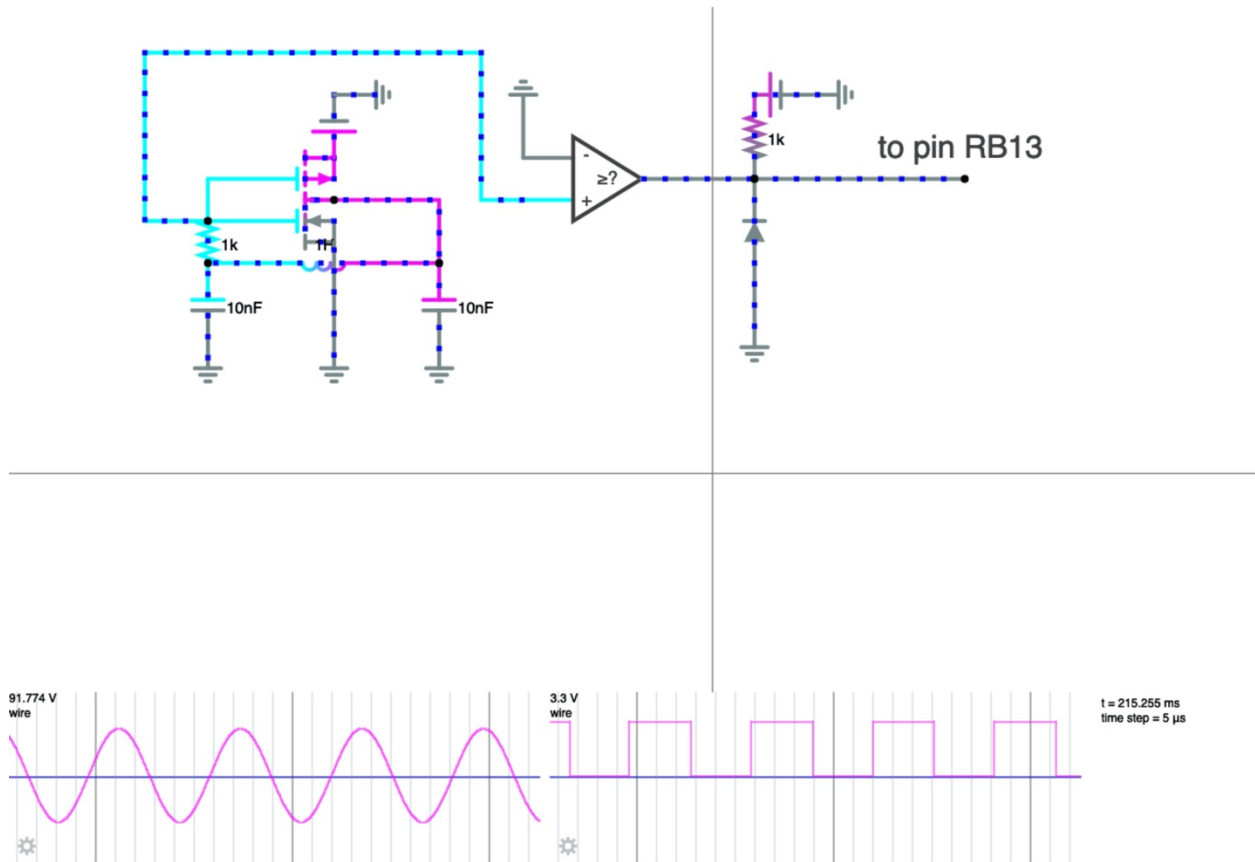


1. Colpitts Oscillator


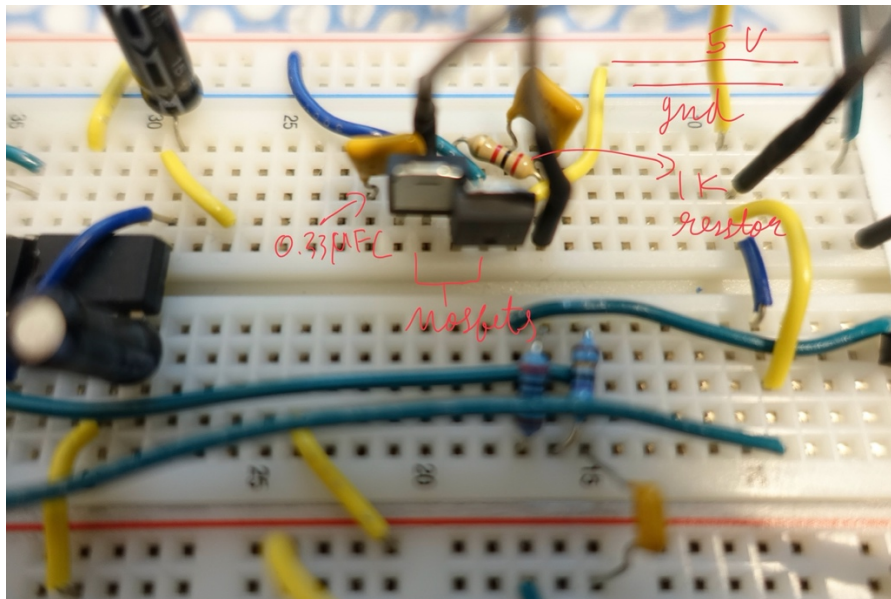


1.1 schematic of the oscillator




1.1 breadboard closeup of the circuit

2.sensor coil

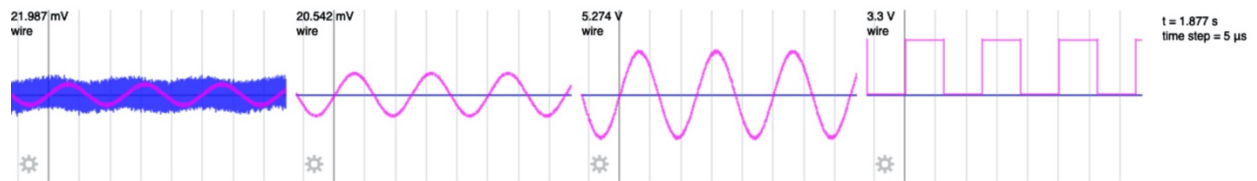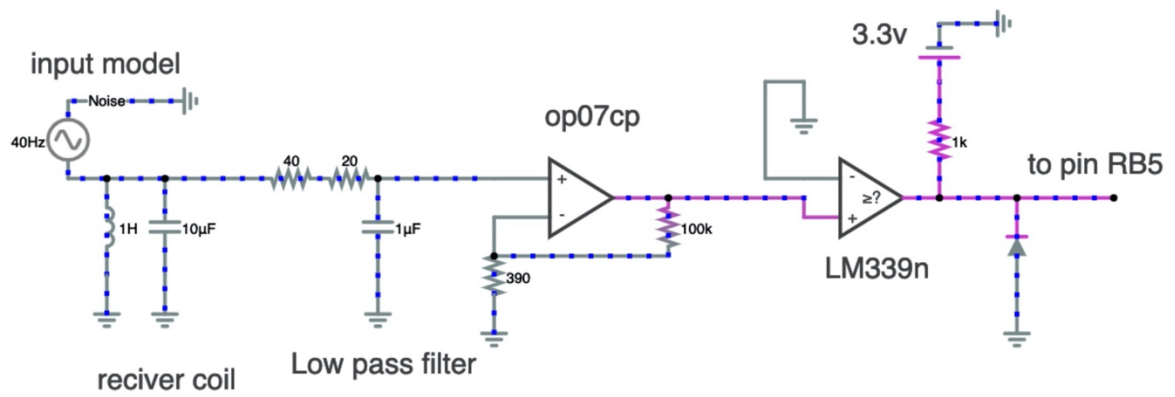


2.1 sensor coil schematic

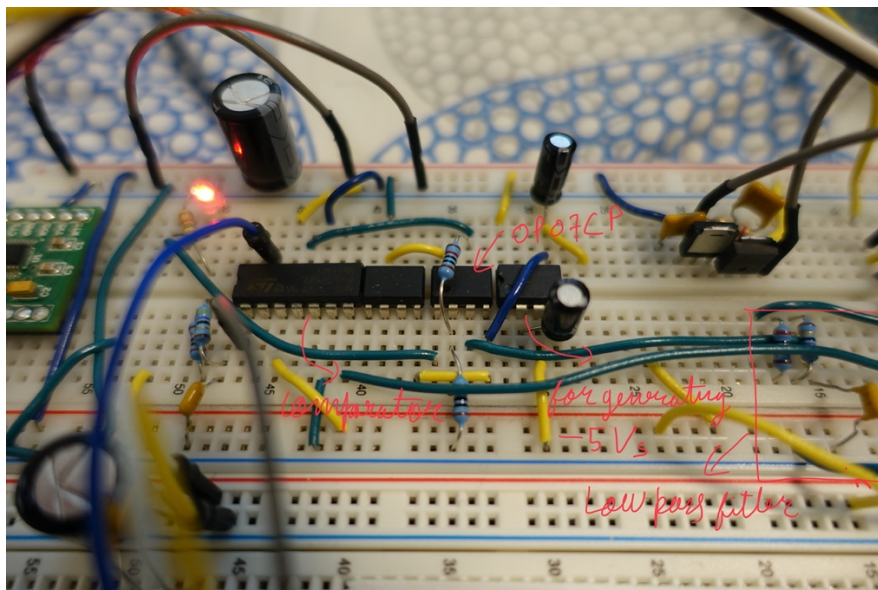


2.1 closeup of the circuit


3. inductor coils

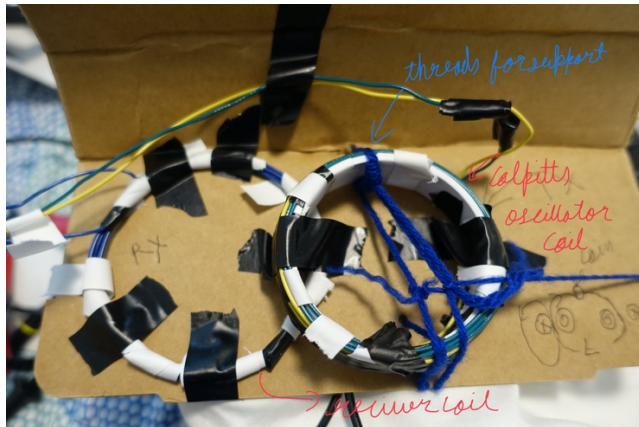

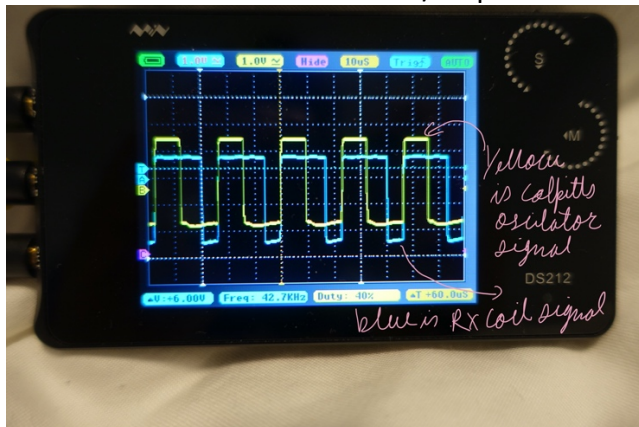3.1 receiver and transmitter coil/Colpitts oscillator coil




3.2 scope with no metal

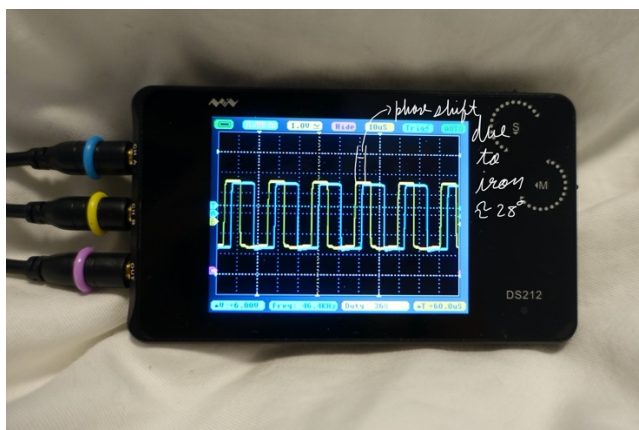


3.3 scope with metal


4. Microcontroller system

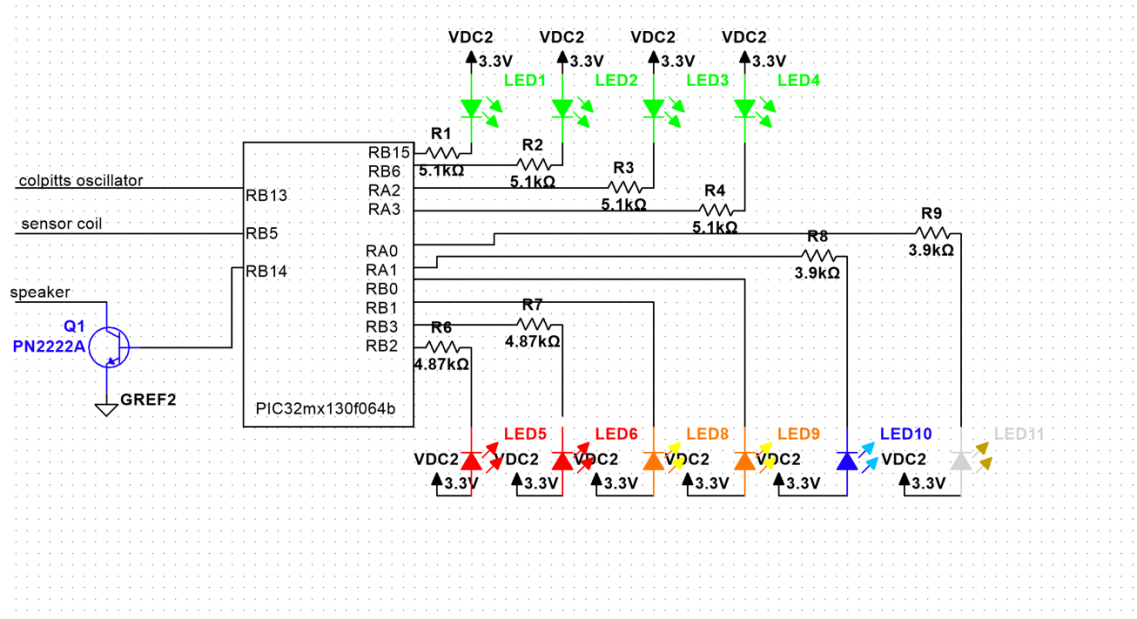

4.1 MCU circuit schematic

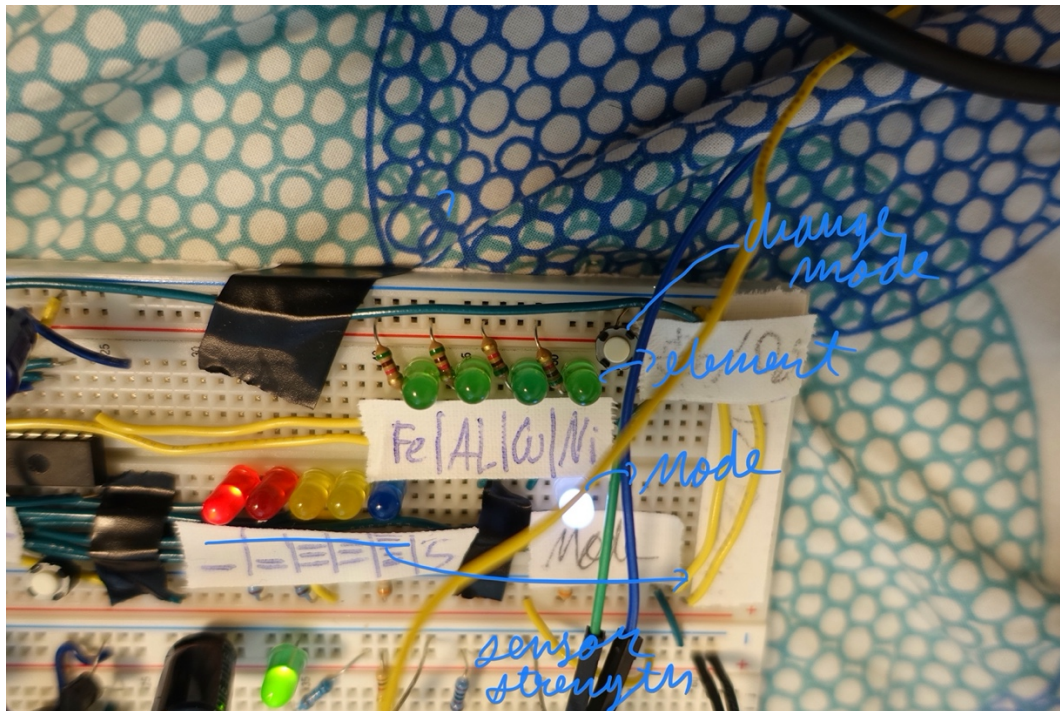


4.2 LED circuit

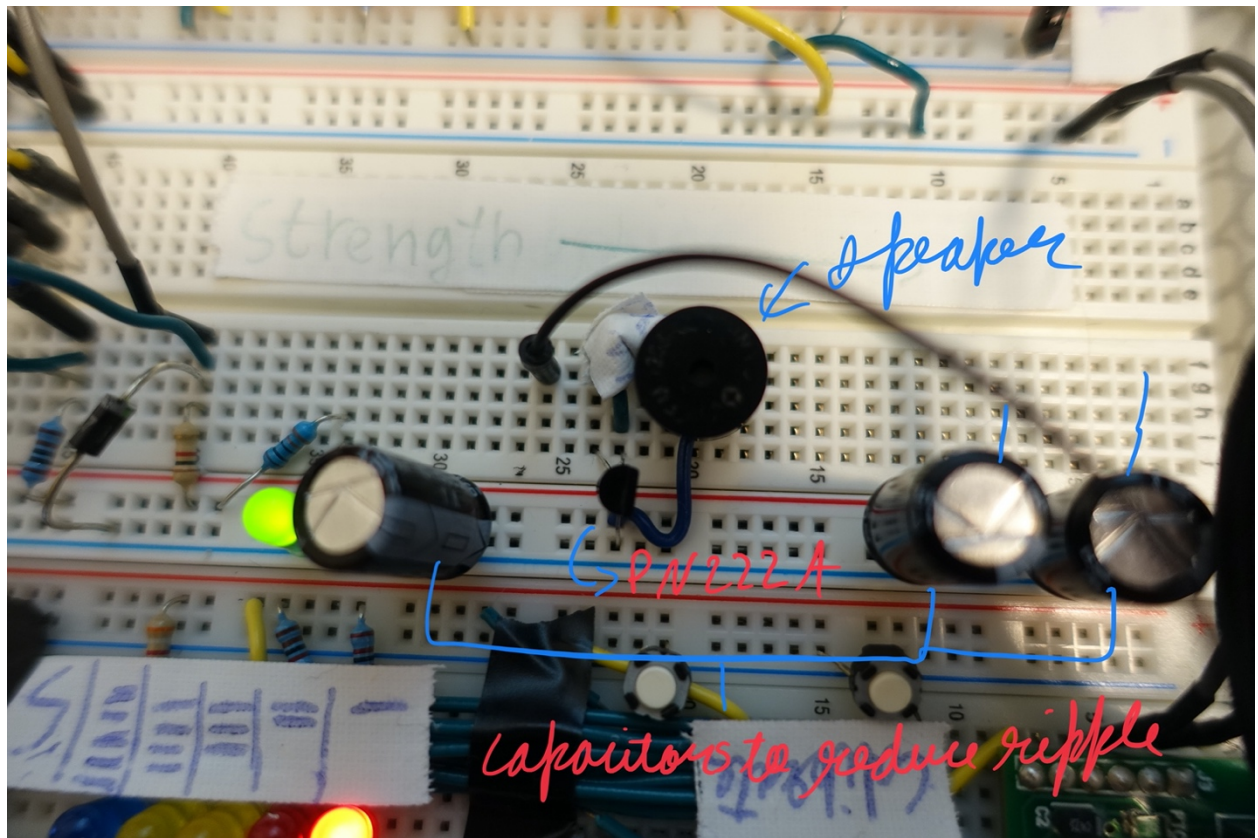


4.3 speaker circuit


4.1.0 modes of operation

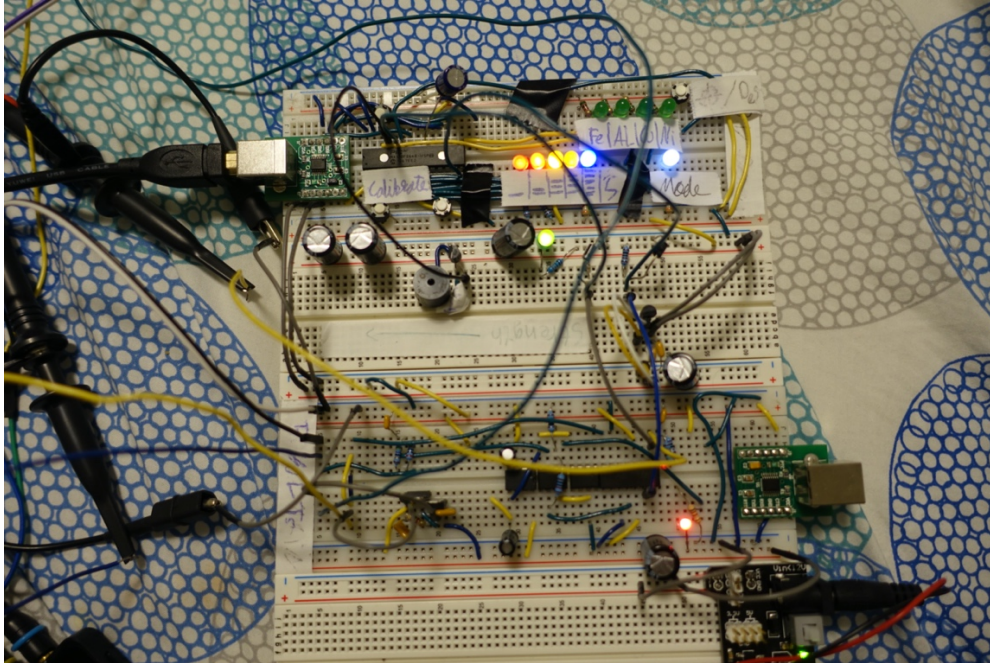

4.1.1 small metal objects detection mode

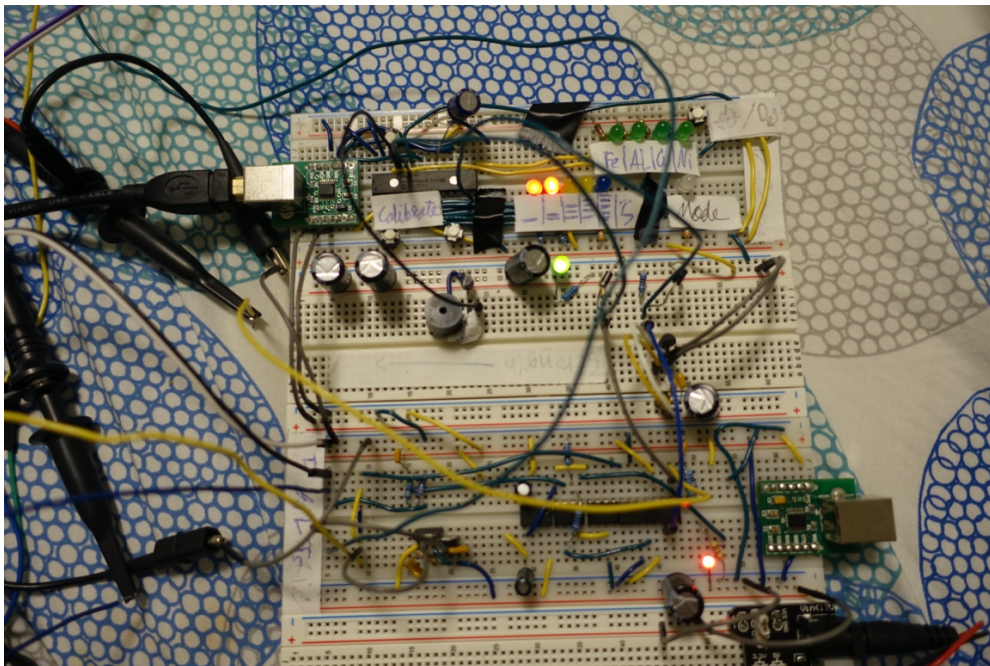

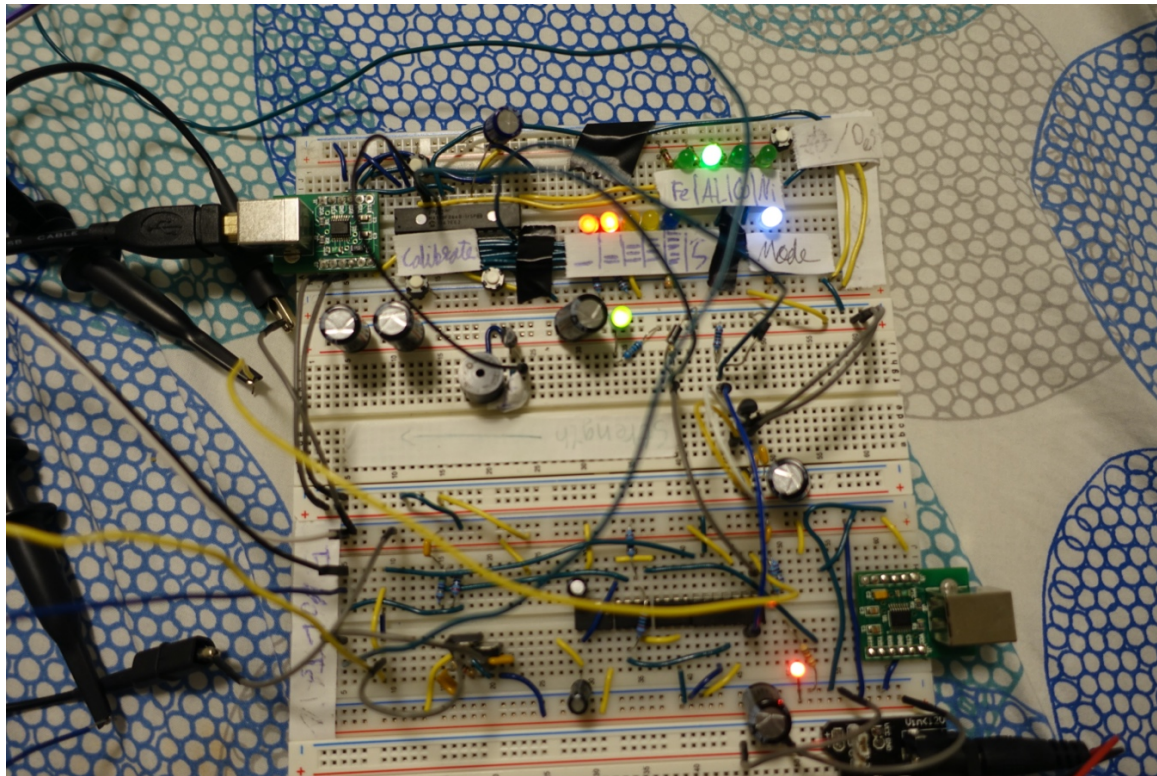
4.1.2 large metal objects detection mode with discrimination



4.1.3 Selective detection mode

5.0 PIC32 system

(from canvas ELEC 291 PIC32_system.pdf)

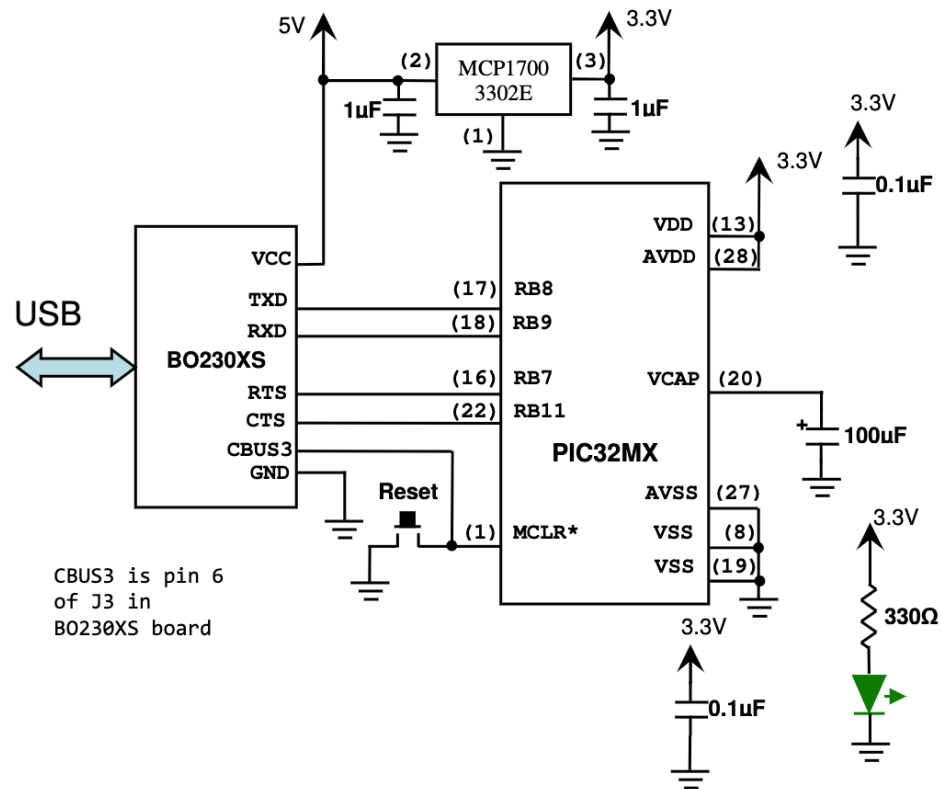

6.0 Parts list

6.1 MCU circuit

- 2x red LED
- 2x yellow LED
- 1x blue LED
- 1x white LED
- 5x green LED

- 4x 5.1k ohm resistor
- 2x 3.9k ohm resistor
- 3x push-buttons
- 1x buzzer
- 1x pn2222A transistor
- 4x 1000uF capacitor
- 2x 1uF capacitor
- 1x 100uF capacitor

- 1x B0X32
- 1x PIC32MX130F064B MCU
- 1x MCP1700

6.2 Colpitts oscillator

- 1x 104G-mosfet
- 1x 2955G-mosfet

- 2x 0.33uF capacitor
- 1x 1k resistor

- 1.5 meter copper wire